

CSE260

Lab Report 02

Section: 03B

Table: 5

Submitted by

23201107 - Sultan Mohammad Farid

23201082 - Muhtasim Fuad

23201416 - Amirun Nahin

23201438 - Ahnaf Hossain Rauf

Experiment # 4 : Design and Implementation of 4-bit Parallel Binary Adder

Experiment # 5 : Implementation of 4-bit Magnitude Comparator

Experiment # 6 : Design circuits using encoder & decoder

Experiment # 7 : Function Implementation using MUX

Required Components for Lab-4:

1. IC 7408
2. IC 7432
3. IC 7486
4. IC 7483

Required components for Lab-5:

1. IC 7408
2. IC 7432
3. IC 7404
4. IC 4077

Required components for Lab-6:

1. IC 74138
2. IC 74148

Required components for Lab-7:

1. IC 74153
2. IC 7408
3. IC 7432
4. IC 7404

The experimental Setup are attached in next pages.

CSF260

Lab-4

Section-3B

Table-5:


23201107

23201416

23201438

23201082

Half Adder Circuit:

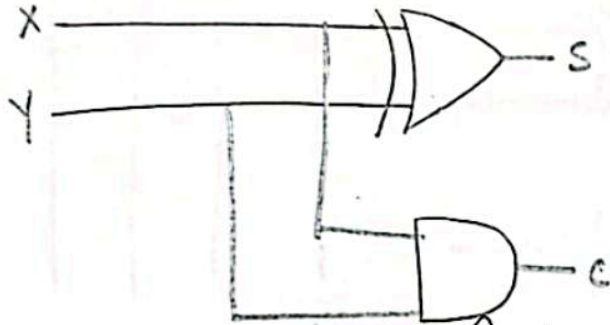


$$S = X \oplus Y$$

$$C = XY$$

*Pratim*  
20.4

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder circuit:

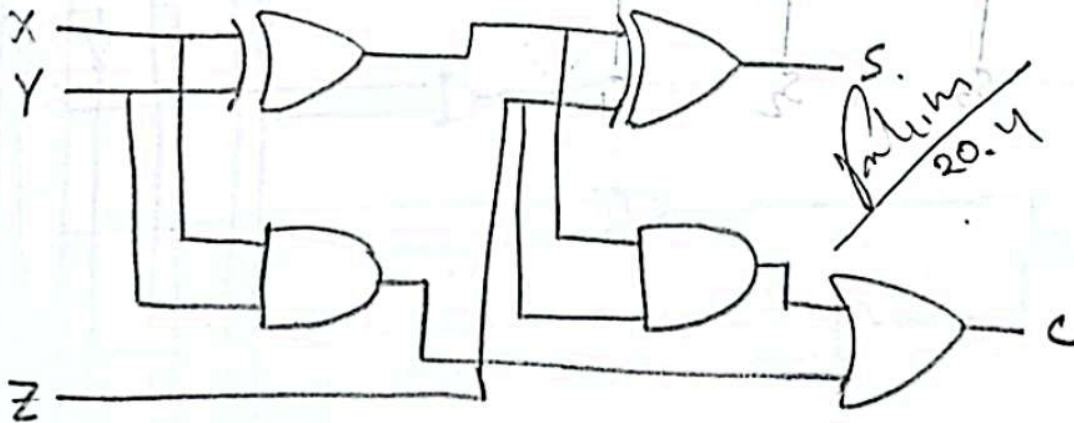


$$C = XY + (X \oplus Y)Z$$

$$S = (X \oplus Y) \oplus Z$$

*Pratim*  
20.4


x	y	z	c	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

A. four-bit Parallel adder circuit:

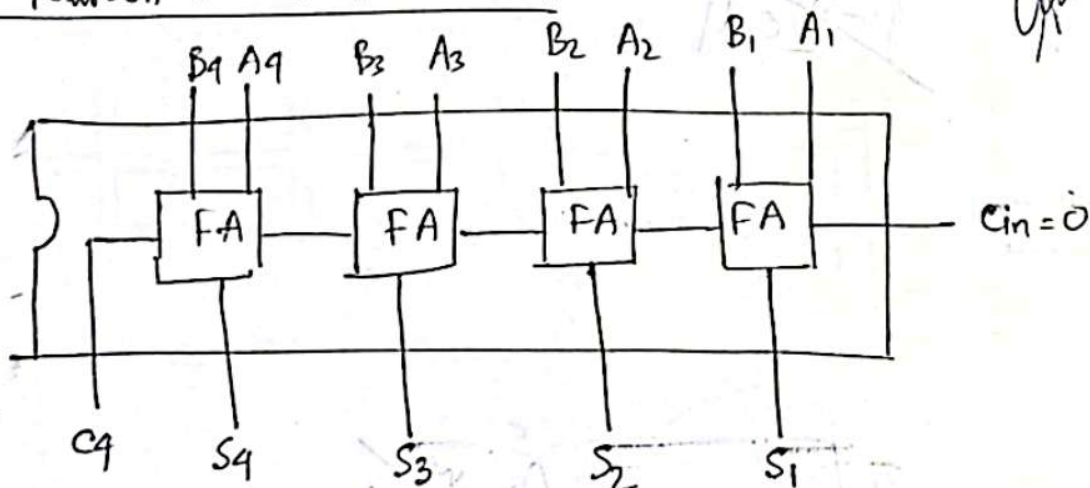


# Experiment 5

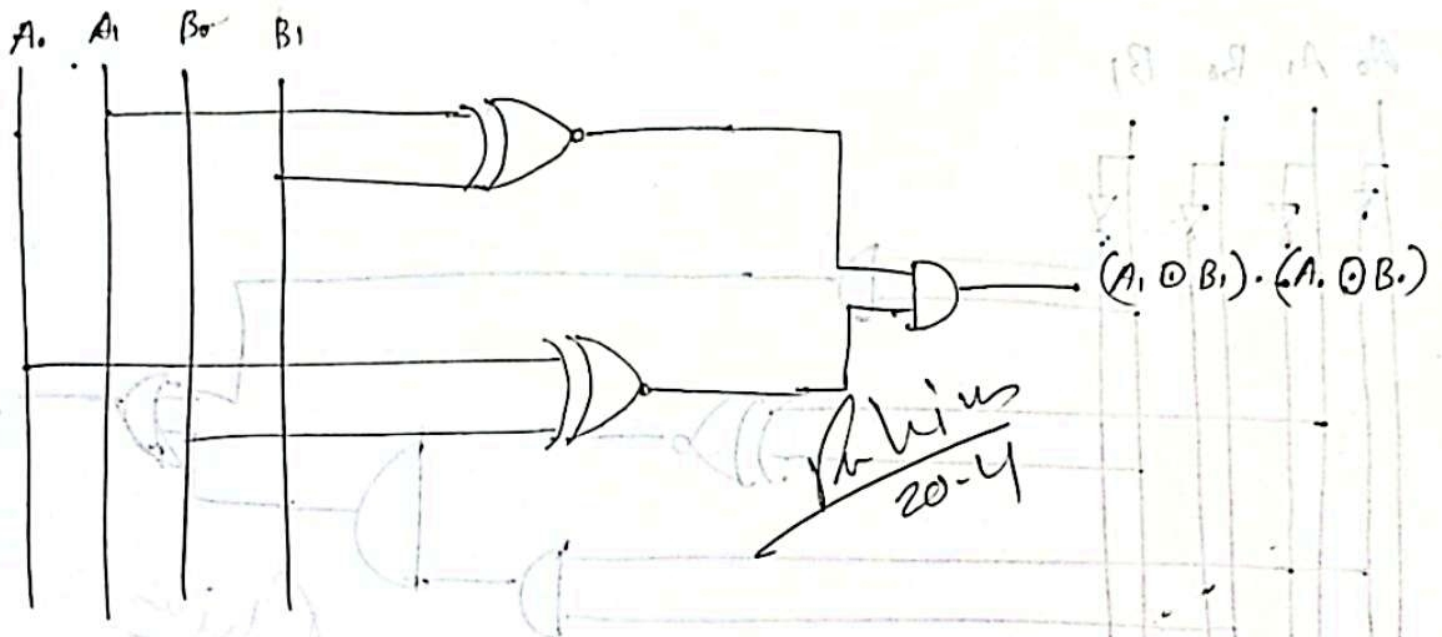1.  $A = B \Rightarrow (A_1 \odot B_1) \cdot (A_0 \odot B_0)$




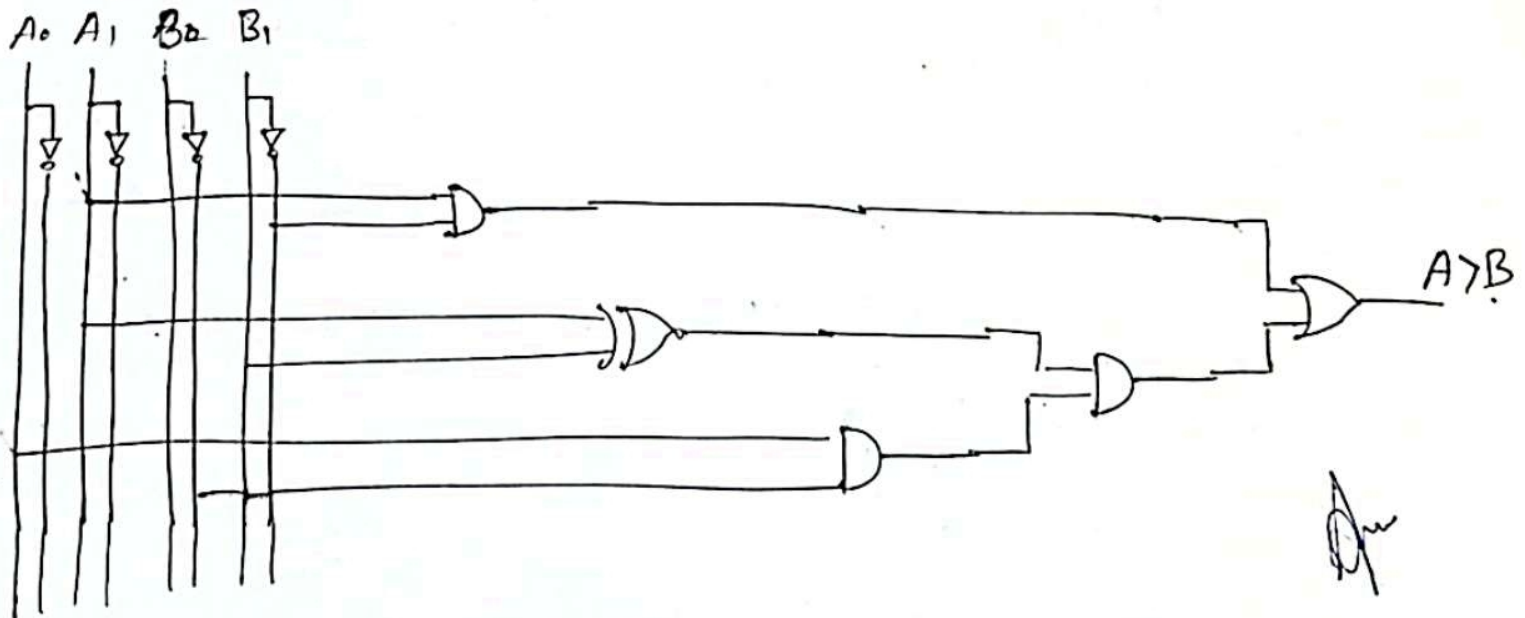2.  $A > B \Rightarrow A_1 B_1' + (A_1 \odot B_1) \cdot A_0 B_0'$



$$3. A < B \Rightarrow A_1' B_1 + (A_1 \odot B_1) \cdot A_0' B_0$$

$A_0 \ A_1 \ B_0 \ B_1$

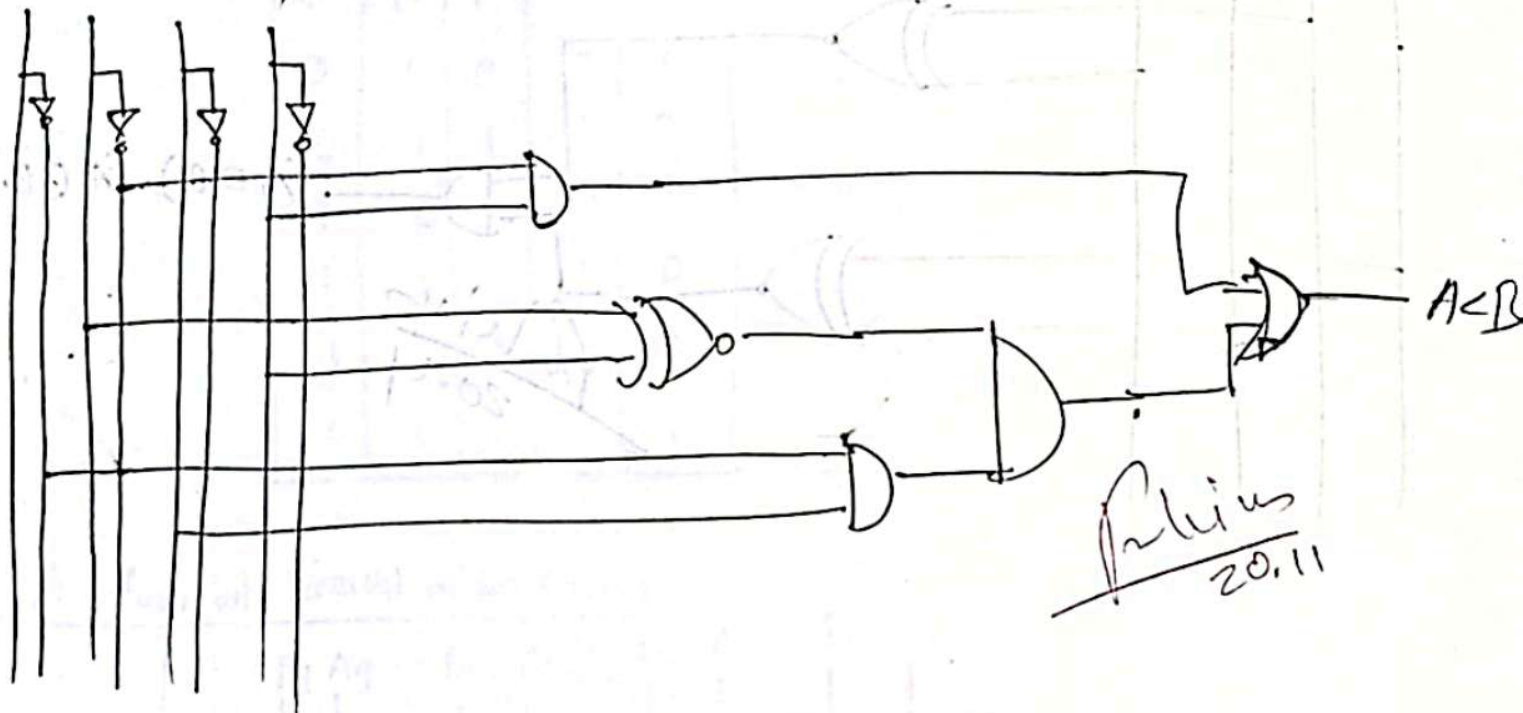


$A < B$



# Experiment - G

11-12-25

23201107  
23201082  
23201916  
23201438

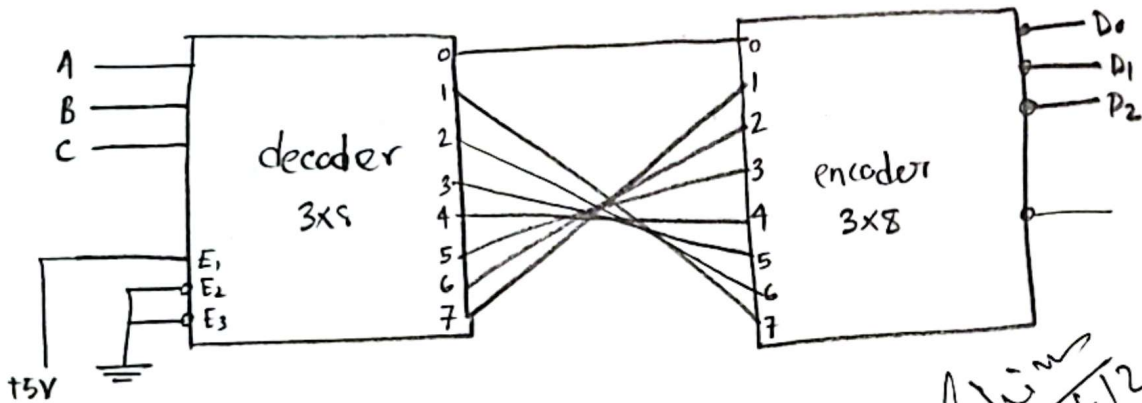

Task 1:

(4x1) MUX:

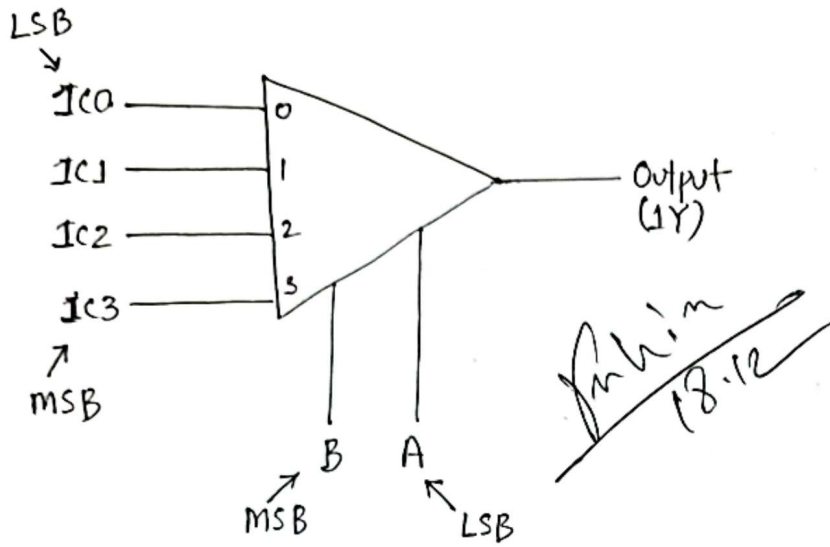


Table-5

23201107
23201416
23201438
23201082

Task 2:

$$F(A, B, C, D) = \sum(1, 2, 3, 4, 5, 6, 7, 9, 11, 12, 13)$$

Table for variable A and B

	I0	I1	I2	I3
A'B'	0	1	2	3
A'B	4	5	6	7
AB'	8	9	10	11
AB	12	13	14	15

$$\therefore I0 = B$$

$$I1 = 1$$

$$I2 = A'$$


$$I3 = A' + B'$$

$$\begin{aligned} &A'B' + AB \\ &= B(A' + A) \\ &= B \end{aligned}$$

$$\begin{aligned} &A'B' + A'B \\ &= A'(B' + B) \\ &= A' \end{aligned}$$
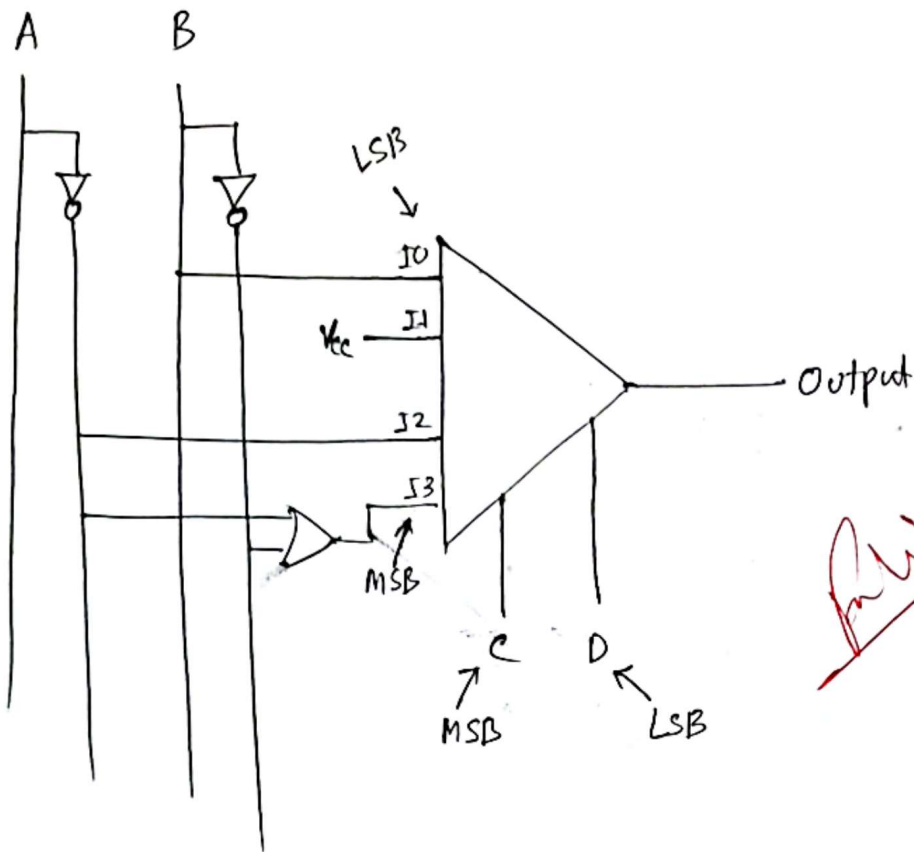
$$\begin{aligned} &A'B' + A'B + AB' \\ &= A'(B' + B) + AB' \\ &= A' + AB' \\ &= (A' + A)(A' + B') \\ &= A' + B' \end{aligned}$$






*Pravin*  
18-12

"Ans. to the ques. no. (1)"


Truth Table:

Inputs				Excess-3 Outputs				
Minterm	A	B	C	Minterm	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	0	0	3	0	0	1	1
1	0	0	1	4	0	1	0	0
2	0	1	0	5	0	1	0	1
3	0	1	1	6	0	1	1	0
4	1	0	0	7	0	1	1	1
5	1	0	1	8	1	0	0	0
6	1	1	0	9	1	0	0	1
7	1	1	1	10	1	0	1	0

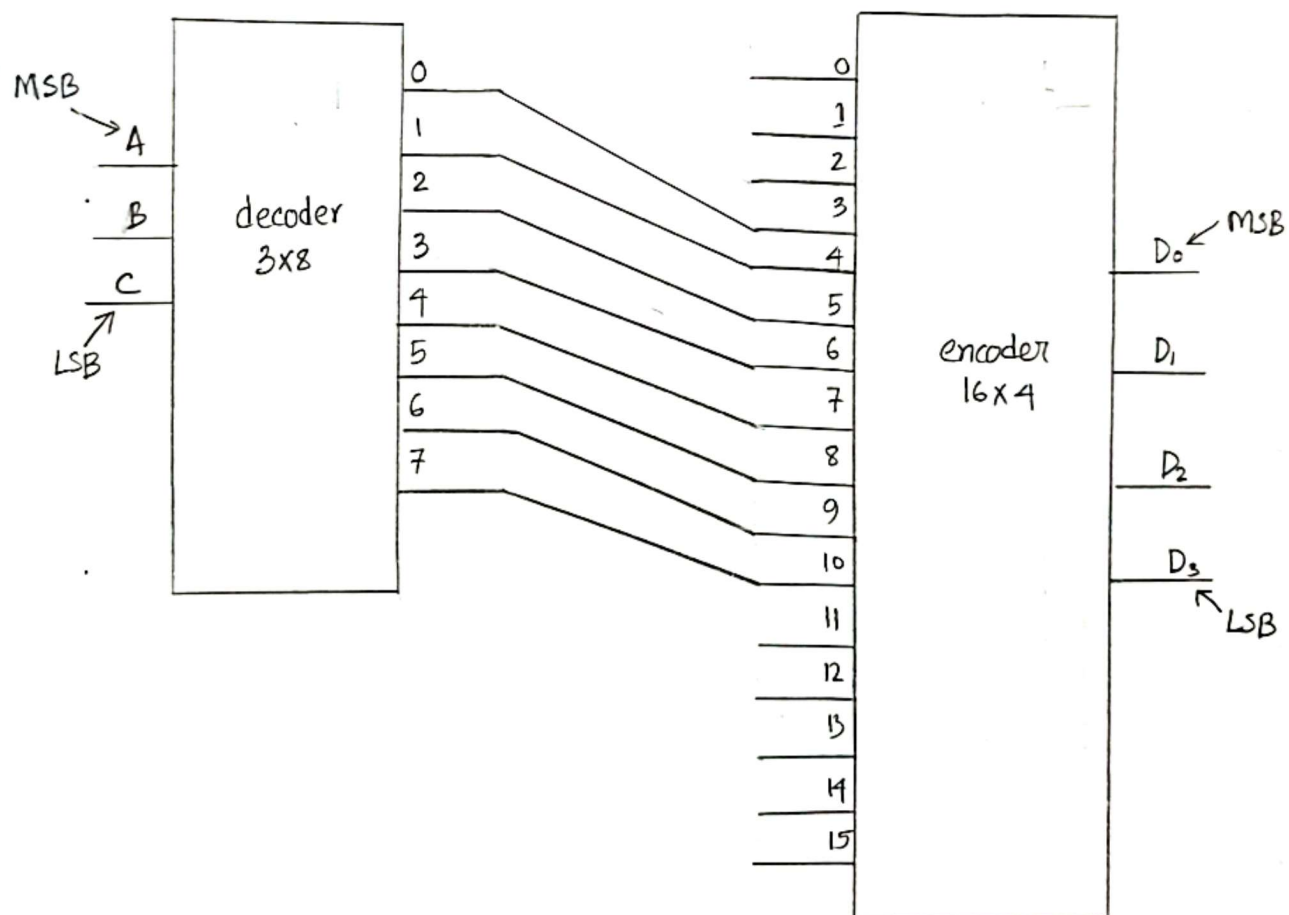

"Ans. to the ques. no. (2)"

B<sub>0</sub>

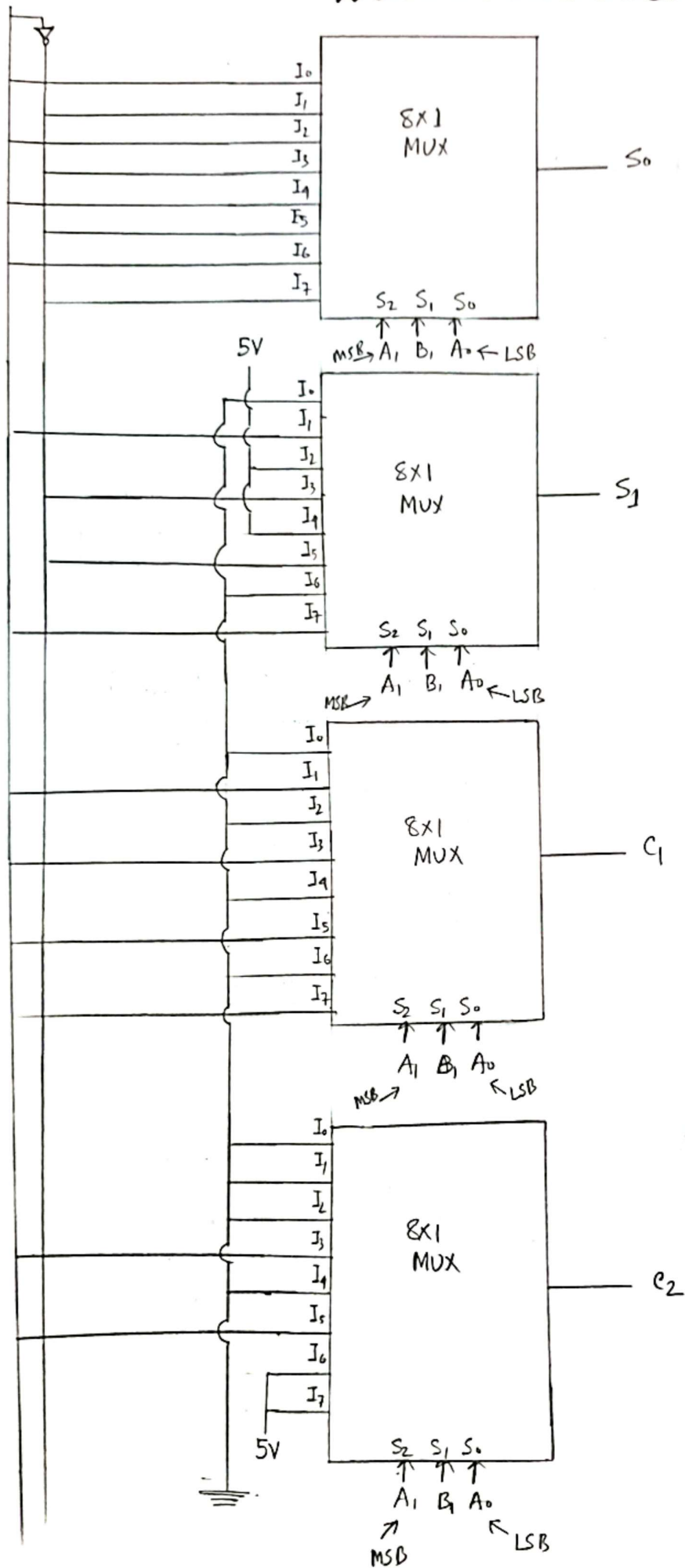

Truth Table:

$A_1$	$B_1$	$A_0$	$B_0$	$S_0$	$S_1$	$C_1$	$C_2$
0	0	0	0	$0/B_0$	0	0	0
0	0	0	1	$1/B_0$	0	0	0
0	0	1	0	$1/B_0'$	$0/B_0$	$0/B_0$	0
0	0	1	1	$0/B_0'$	$1/B_0$	$1/B_0$	0
0	1	0	0	$0/B_0$	1	0	0
0	1	0	1	$1/B_0$	1	0	0
0	1	1	0	$1/B_0'$	$1/B_0'$	$0/B_0$	$0/B_0$
0	1	1	1	$0/B_0'$	$0/B_0'$	$1/B_0$	$1/B_0$
1	0	0	0	$0/B_0$	1	0	0
1	0	0	1	$1/B_0$	1	0	0
1	0	1	0	$1/B_0'$	$1/B_0'$	$0/B_0$	$0/B_0$
1	0	1	1	$0/B_0'$	$0/B_0'$	$1/B_0$	$1/B_0$
1	1	0	0	$0/B_0$	0	0	1
1	1	0	1	$1/B_0$	0	0	1
1	1	1	0	$1/B_0'$	$0/B_0$	$0/B_0$	1
1	1	1	1	$0/B_0'$	$1/B_0$	$1/B_0$	1