

' Assignment - 03 '

Amirun Nahin

ID: 23201416

Sec: 03-B

Course: CSE 260

Semester: Fall 2025


Date : 19-12-2025

Answer to the question no-01

Truth Table for 1's complement number system:

	A	B	C	D ₂	D ₁	D ₀	
0	0	0	0	1	1	1	7
1	0	0	1	1	1	0	6
2	0	1	0	1	0	1	5
3	0	1	1	1	0	0	4
4	1	0	0	0	1	1	3
5	1	0	1	0	1	0	2
6	1	1	0	0	0	1	1
7	1	1	1	0	0	0	0

The circuit,

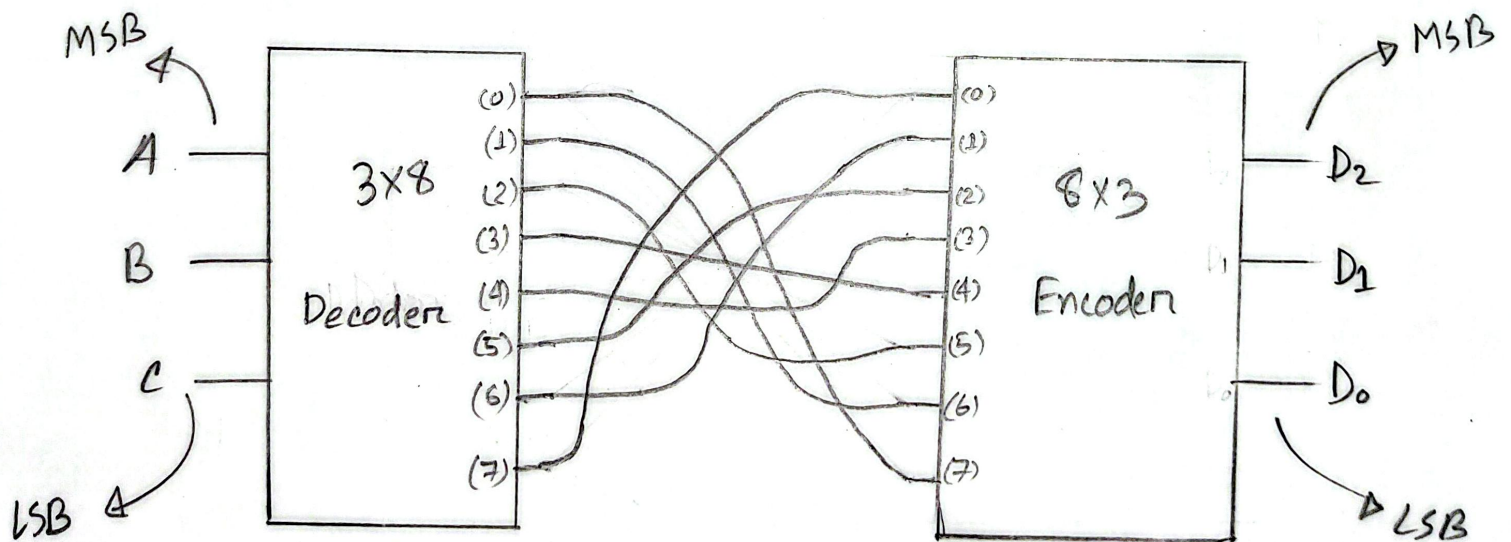

Ans. to the question no-02

Given function,


$$F(A, B, C, D) = \sum (0, 1, 2, 7, 8, 10, 11, 13, 15)$$

We can use four 2:1 MUX(s) and one 4:1 MUX to implement the following function.

So,

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	A'	1	A	0	A	0	1


Building the diagram,

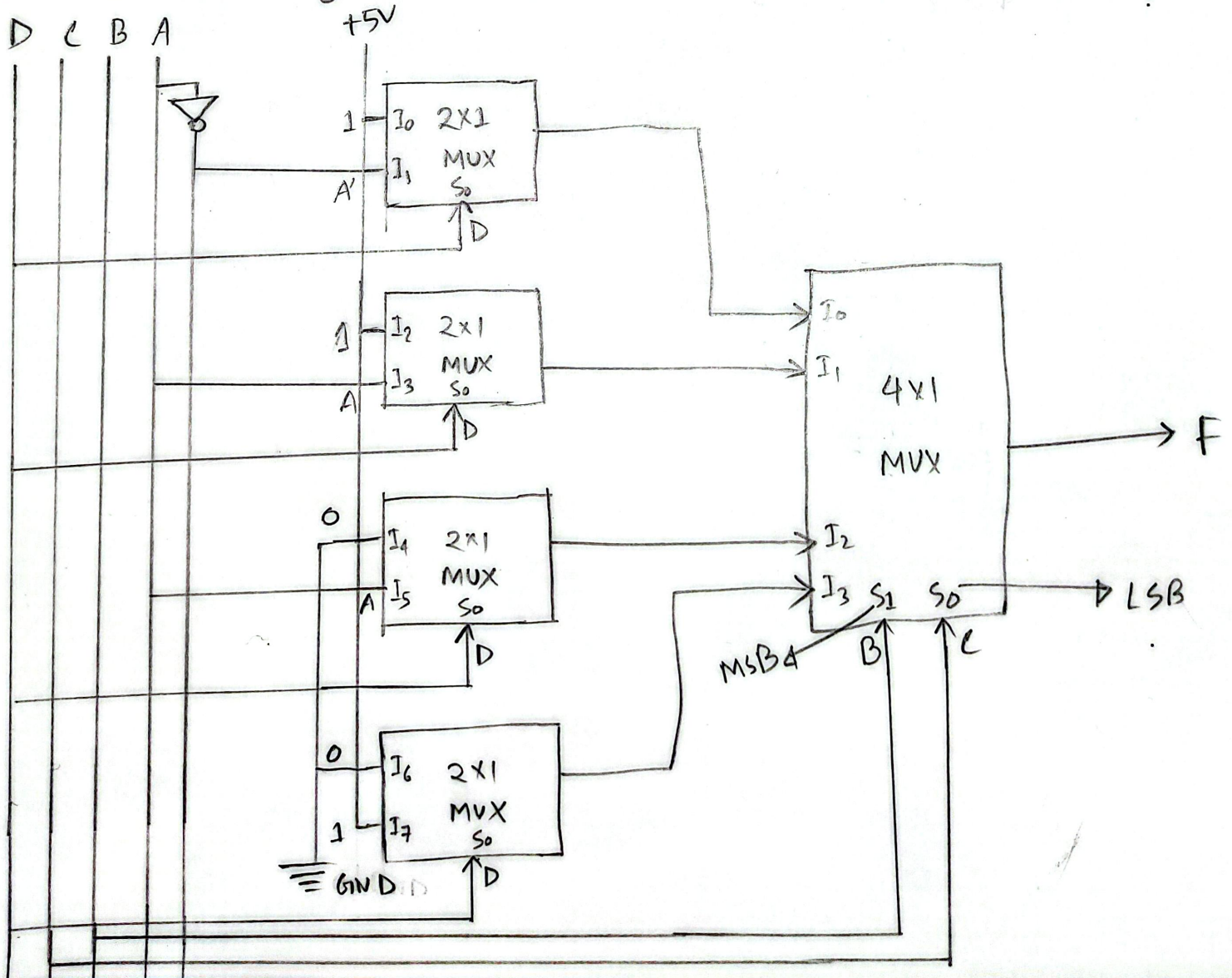

Ans. to the question no-03

Designing the given circuit using 4bit Parallel Adder Cum Subtractor;

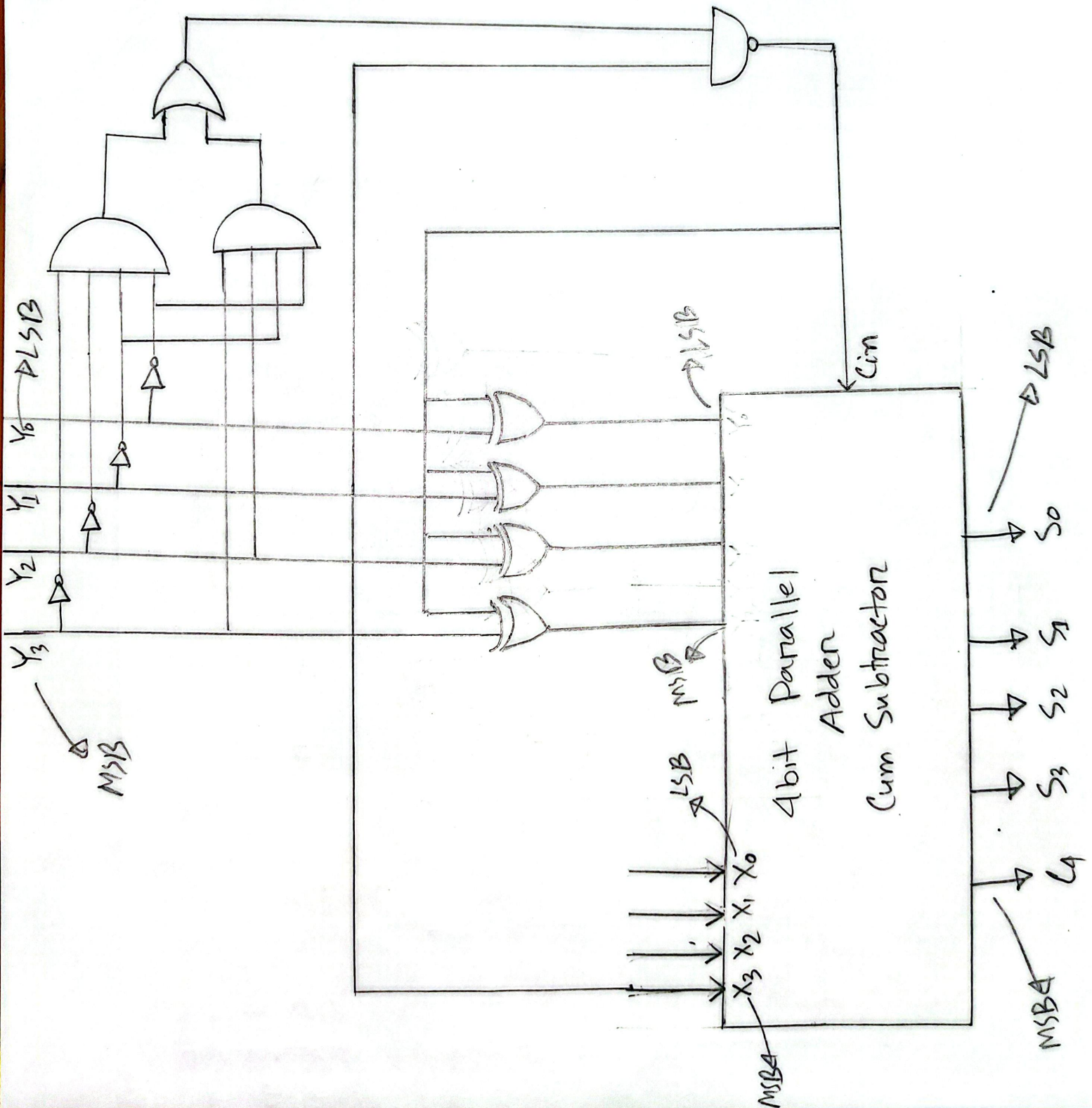To be greater than or equal to 8, MSB of X has to be 1 and, to be divisible by 12, SOP has to be, $Y_3'Y_2'Y_1'Y_0'$ or $Y_3Y_2Y_1Y_0'$. So, the circuit will look like this;



Ans. to the question no-04

Designing a 13 person voting system.

