

Experiment # 3: Parity Bit Checker and Generator

Objective:


- To design and implement an even parity Generator and even parity checker using XOR gates. (IC-7486).

Required Components:

 
1. IC 7486 \times 1

Diagrams:

Building an even parity generator using XOR Gates for 4-bit Data:



 Building an even parity checker using XOR Gates for 4-bit Data:



Procedure:

- Construct the Circuits of both the parity bit generator and checker on the breadboard.
- Remember that each IC's pin 14 is connected to the "+5V" position of the DC Power Supply of AT-700, and pin 7 is connected to the "GND" position.
- Connect the inputs to the Data switches and outputs to any position of the LED Display.

Result:

Complete both of the following truth tables.

Truth Table for Parity Bit Generator:

	Data				Parity
	D ₃	D ₂	D ₁	D ₀	
a.	1	0	0	1	
b.	0	0	0	1	
c.	1	1	1	1	
d.	0	0	0	0	

Truth Table for Parity Bit Checker:

	Data					Error
	Parity	D ₃	D ₂	D ₁	D ₀	
a.	1	1	0	0	1	
b.	0	0	0	0	1	
c.	0	1	1	1	1	
d.	1	0	0	0	0	